

Simplified Overdrive Wiring and Warning Light

By Steve Byers

This is my version of the wiring diagram for the overdrive. I put it together for my own better understanding of how the electrical system of the overdrive works, and as a troubleshooting aid. I have done some modifications to my overdrive electrical system, and this is the schematic for that. The mods are the 20A fuse and the overdrive "warning" light.

